



Department of Electrical & Electronic Engineering

EEE 447 – Power Electronics

PROJECT

Design and Simulation of a Buck Converter.

Course Instructor : Dr Ratil Hasnat

Group – 3

Student Name	Student ID
Sakib Hasan Mitul	2020-1-80-092
Debabrata Roy	2021-1-80-022

Date of Submission – 21st January 2025

OBJECTIVE

To design and simulate a DC-DC Buck Converter that steps down an input voltage to a specified output voltage and analyze its performance under varying load conditions.

THEORY

A buck converter, also known as a step-down converter, is a DC-DC power converter that reduces the input voltage to a lower, regulated output voltage while maintaining energy efficiency. It works by switching a semiconductor device (like a MOSFET or transistor) at high frequency, transferring energy through an inductor to the load. The inductor and capacitor in the circuit act as energy storage elements, smoothing out the output voltage and current. The basic operation relies on Pulse Width Modulation (PWM) to control the duty cycle, which directly determines the output voltage:

$$V_{out} = D \times V_{in}$$

Where D is the duty cycle (ratio of the ON time to the total switching period). The key advantages of buck converter are high efficiency, compact size and adaptability for various applications in power supplies and battery-operated devices.

EQUIPMENT LIST

- 1) MOSFET (IRFZ44N)
- 2) Capacitor (10uF)
- 3) Inductor (30uH)
- 4) Resistor (1k Ω)
- 5) Signal generator
- 6) Oscilloscope
- 7) DC voltage source

THEORITICAL ANALYSIS

Given specification for design

- *Input Voltage:* $V_{in} = 24\text{ V}$
- *Output Voltage:* $V_{out} = 12\text{ V}$
- *Load Resistance:* $R = 10\ \Omega$
- *Switching Frequency:* $f_s = 50\text{ kHz}$

$$\text{Duty cycle, } D = \frac{V_{out}}{V_{in}} = \frac{12\text{ V}}{24\text{ V}} = 0.5$$

$$\text{Time period, } T = \frac{1}{f_s} = \frac{1}{(50 * 10^3)} = 20\mu\text{s}$$

$$D = \frac{t_{on}}{T}$$

$$t_{on} = D * T$$

$$T = t_{on} + t_{off}$$

$$t_{off} = T - t_{on}$$

$$= T - D * T$$

$$= T * (1 - D)$$

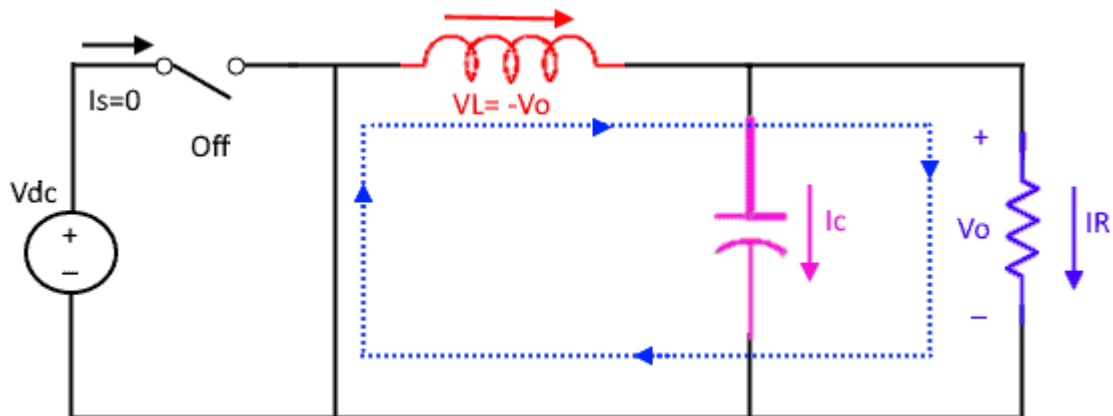


Fig 1: Buck converter when switch is open

Here,

$$V_L = -V_o$$

$$V_L = L * \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{VL}{L}$$

The change in current during off period (ΔI_{off}) is; $[\Delta I_{off} = I_{max} - I_{min}]$

$$\Delta I_{off} = (VL/L) * t_{off}$$

$$\Delta I_{off} = (-V_o/L) * (1 - D)T$$

$$\Delta I_{off} = (V_o/L) * (1 - D)T$$

$$I_{max} - I_{min} = (V_o/L) * (1 - D)T \text{ -----(i)}$$

Here,

$$I_o = V_o/RL$$

$$= (I_{max} + I_{min})/2$$

$$I_{max} + I_{min} = 2I_o = 2 * V_o/RL \text{ -----(ii)}$$

After (ii - i) we get,

$$2I_{min} = 2V_o/RL - V_o/L * (1 - D)T$$

$$I_{min} = V_o/RL - V_o/2L * (1 - D)T$$

For BCM,

$$I_{min} = 0$$

So,

$$V_o/RL - V_o/2L_c * (1 - D)T = 0$$

$$L_c = (RL/2) * (1 - D)T$$

$$= (RL/2fs) * (1 - D)$$

$$= (10\Omega/2 * 50 * 10^3) * (1 - 0.5)$$

$$= 50\mu H$$

As for CCM

$$L > L_c$$

We are taking $L = 100\mu H$

Combining (i + ii) we get,

$$2I_{max} = 2V_o/RL + V_o/L * (1 - D)T$$

$$\begin{aligned} I_{max} &= V_o * [1/RL + (1 - D)/2 * L * fs] \\ &= 12 * [1/10\Omega + (1 - 0.5)/2 * 100 * 10^{-6} * 50 * 10^3] \\ &= \mathbf{1.8A} \end{aligned}$$

$$\begin{aligned} I_{min} &= V_o/RL - V_o/2L * (1 - D)T \\ &= (12/10) - (12/2 * 100 * 10^{-6}) * (1 - 0.5) * 20 * 10^{-6} \\ &= \mathbf{0.6A} \end{aligned}$$

$$\begin{aligned} I_L &= I_{max} + I_{min} / 2 \\ &= 1.8 + 0.6 / 2 \\ &= \mathbf{1.2A} \end{aligned}$$

$$\begin{aligned} \text{Inductor ripple current, } \Delta I_L &= 1 - D/L * fs \\ &= 1 - 0.5/(100 * 10^{-6}) * (50 * 10^3) \\ &= \mathbf{0.1A} \end{aligned}$$

Switch (MOSFET) rating [when closed]

$$\begin{aligned} V_{switch_max} &= V_{inmax} + \text{Diode's Forward Biased voltage drop} \\ &= 24 + 0.7V \\ &= 24.7V \text{ (rating should be 20\% higher)} \end{aligned}$$

$$V_{switch_max_rating} = (24.7 + 24.7 * 0.2) = 29.64V \approx \mathbf{30V}$$

$$\begin{aligned} I_{switch_max} &= I_L * D \\ &= 1.2 * 0.5 \\ &= \mathbf{0.6A} \end{aligned}$$

Diode rating [when switch is open]

$$\begin{aligned} V_{RRM} &= V_{inmax} + V_{SW} \\ &= 24 + 0.7 \\ &= 24.7V \text{ (rating should be 20\% higher)} \end{aligned}$$

$$V_{PRM_rating} = (24.7 + 24.7 * 0.2) = 29.64V \approx \mathbf{30V}$$

$$\begin{aligned}
 I_{diode_max} &= I_L * (1 - D) \\
 &= 1.2 * (1 - 0.5) \\
 &= \mathbf{0.6A}
 \end{aligned}$$

*Electrolytic DC **capacitor** selection*

Let's assume that

Ripple percentage, $\Delta V_o/V_o = 2\%$

Here,

$$\begin{aligned}
 \Delta Q &= \frac{1}{2} * (I/2) * (\Delta I/2) \\
 &= (1/2) * (I/2) * (1/2) * ((V_{in} - V_o)/L) * D * T \\
 &= (1/2) * (I/2) * (1/2) * ((\Delta V_o)/L) * (1 - D) * T \\
 \Delta Q &= (1/8) * T^2 * (V_o/L) * (1 - D) \\
 \Delta V_o * C &= (1/8) * T^2 * (V_o/L) * (1 - D) \\
 C &= V_o * (1 - D) / 8 * L * f_s^2 * \Delta V_o \\
 &= (1 - D) / 8 * L * f_s^2 * (\Delta V_o/V) \\
 &= (1 - 0.5) / 8 * (100 * 10^{-6}) * (50 * 10^3)^2 * 0.02 \\
 &= \mathbf{12.5\mu F}
 \end{aligned}$$

$$\begin{aligned}
 \text{Ripple voltage, } \Delta V_o &= 0.02 * 12 \\
 &= \mathbf{0.04V}
 \end{aligned}$$

$$\begin{aligned}
 \text{Voltage rating for capacitor, } V_{cmax} &= V_o + (\Delta V_o/2) \\
 &= 12 + (0.04/2) \\
 &= 12.02V \text{ (rating should be 20\% higher)}
 \end{aligned}$$

$$\begin{aligned}
 V_{cmax_rating} &= V_{cmax} + V_{cmax} * 0.2 \\
 &= 12.02 + 12.02 * 0.2 \\
 &= 14.424V \approx \mathbf{15V}
 \end{aligned}$$

SIMULATION PART

Circuit diagram designed on LTSPICE

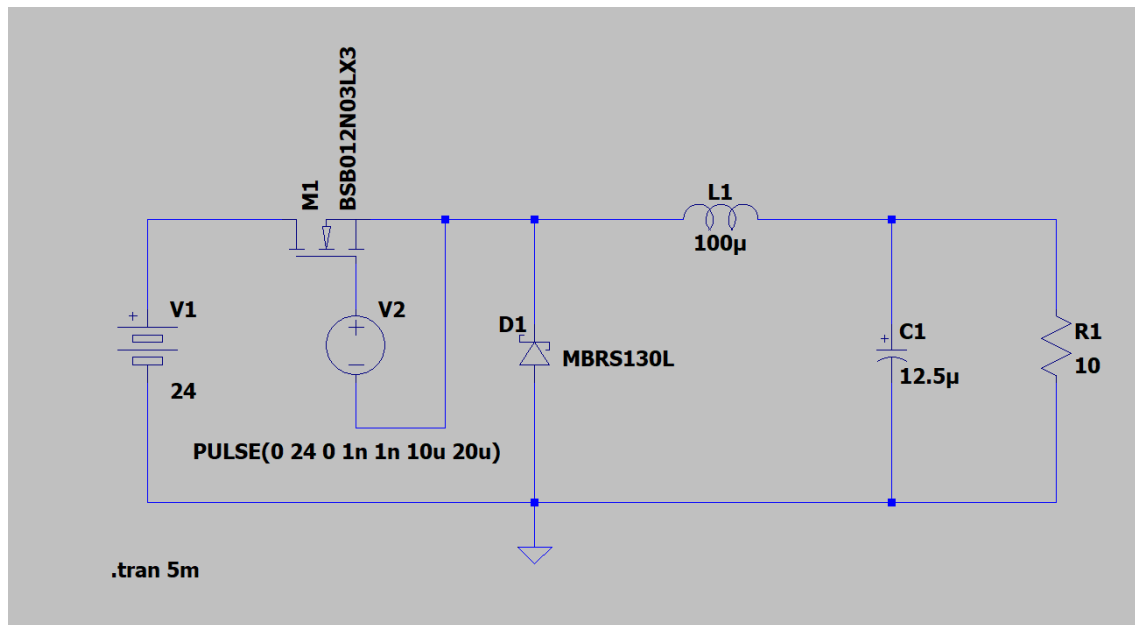


Fig 2: Circuit diagram of the buck converter

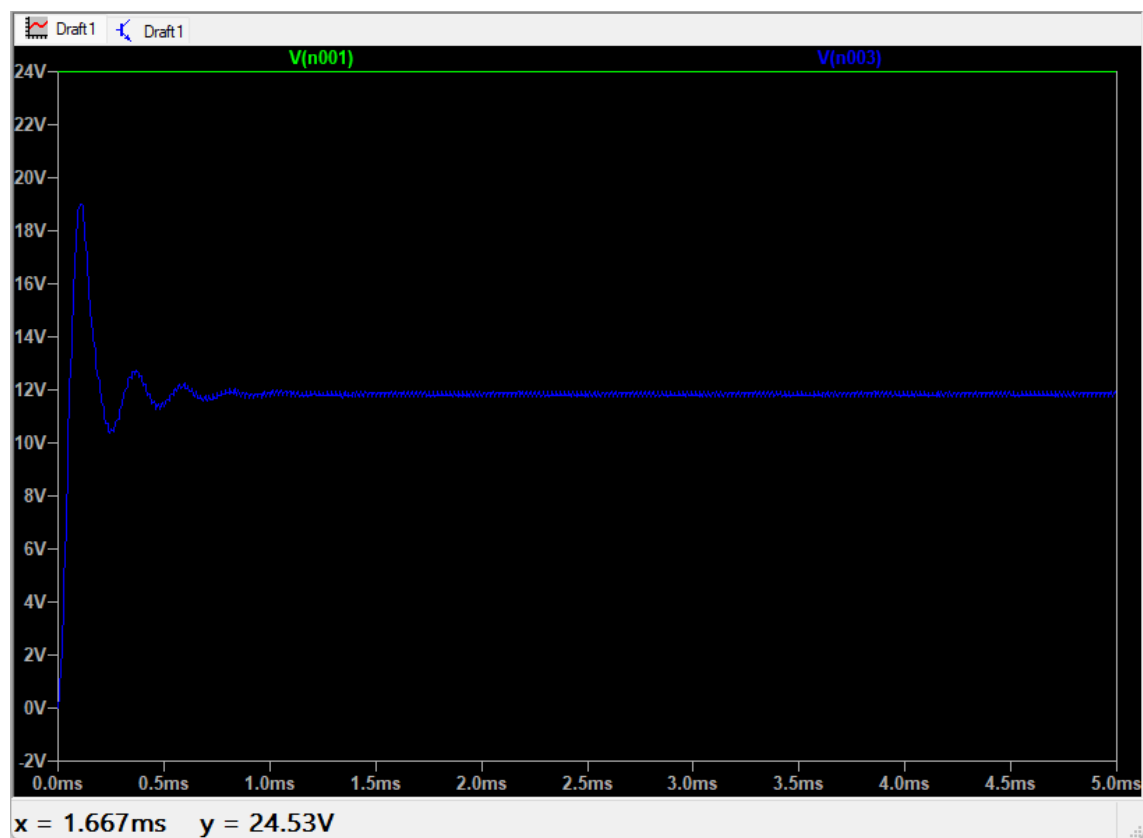


Fig 3: Input (24V) and output (12) voltage waveforms

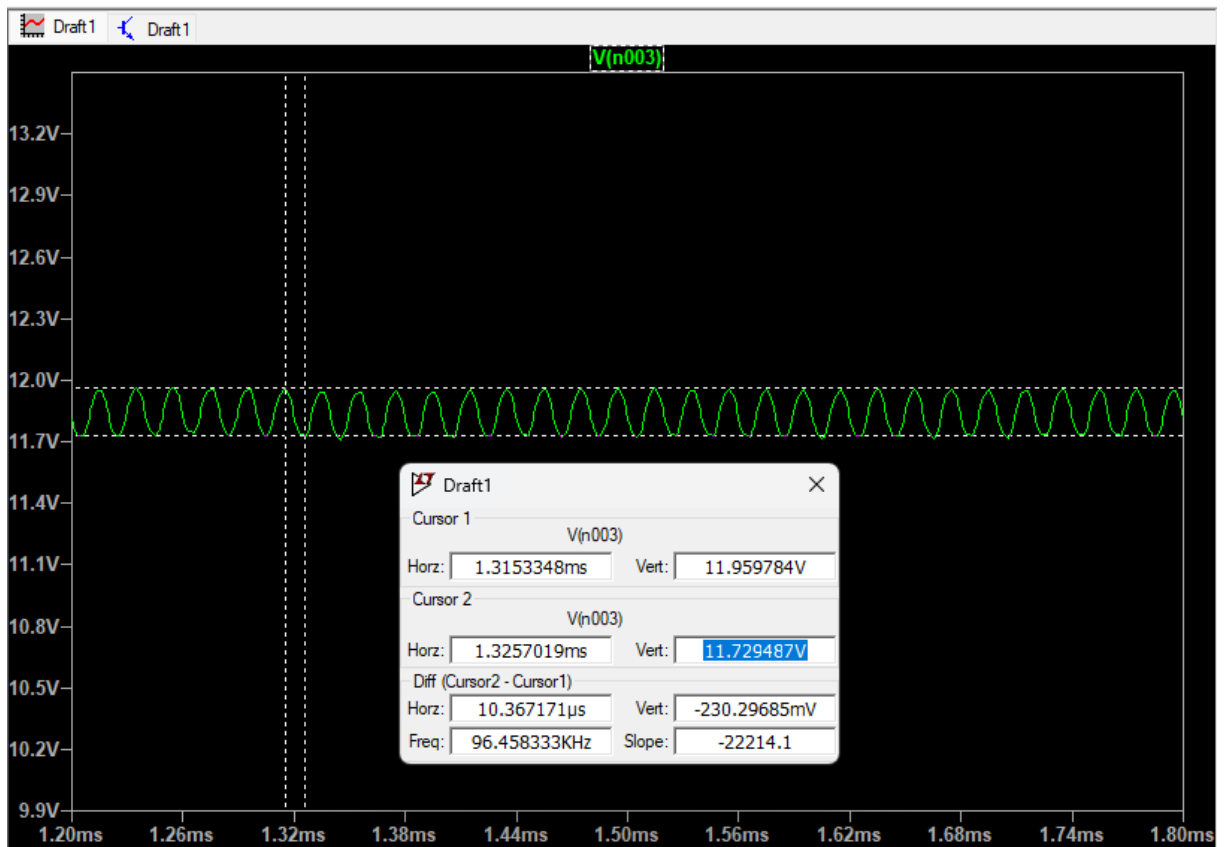


Fig 4: Output voltage waveform

From the graph we can find the ripple voltage, $\Delta V_o = (11.959 - 11.729)V$
 $= 0.23V$

So the ripple percentage we get, $\Delta V_o/V_o = (0.23/11.959) * 100$
 $= 1.92\%$

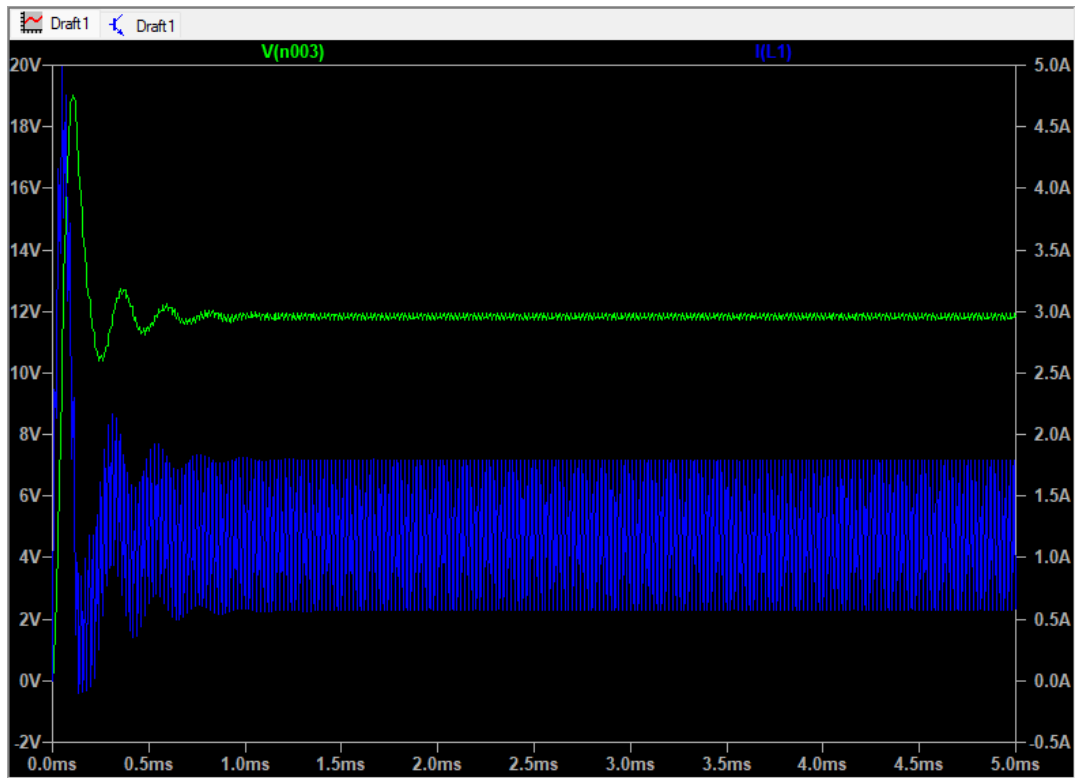


Fig 5: Voltage ripple vs Inductor current waveform

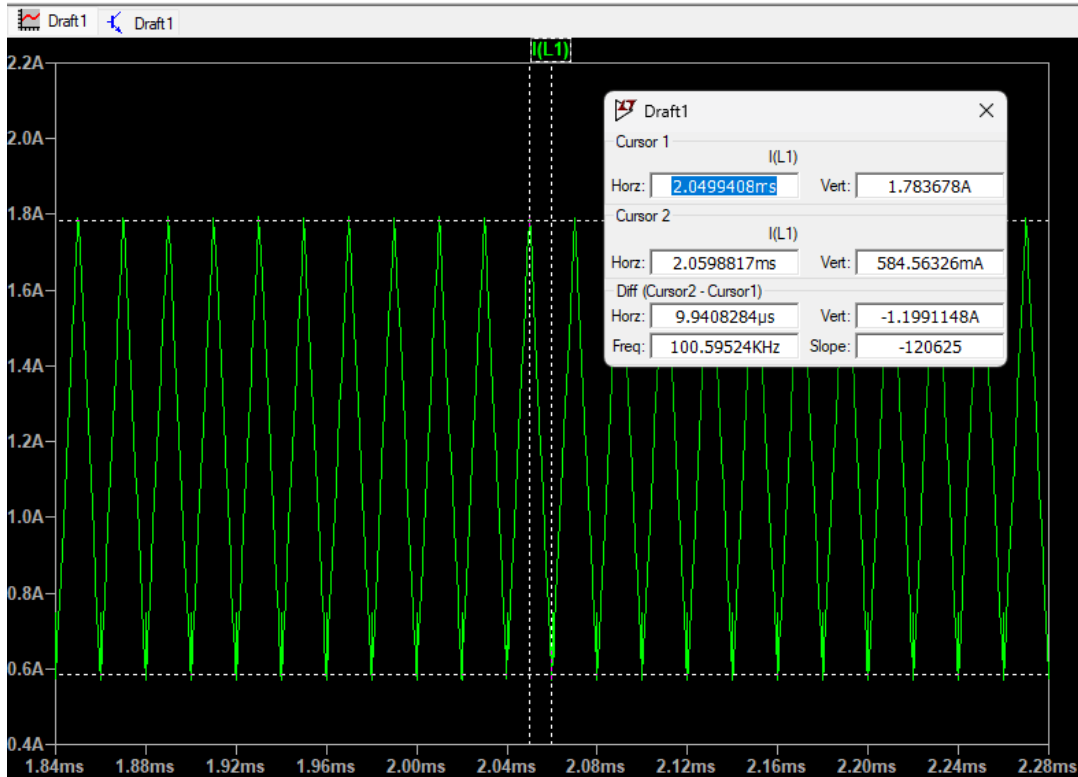


Fig 6: Inductor current waveform

From the graph we can find the inductor current, $I_L = (1.783678 + 0.5845632)/2A$
 $= 1.184A$

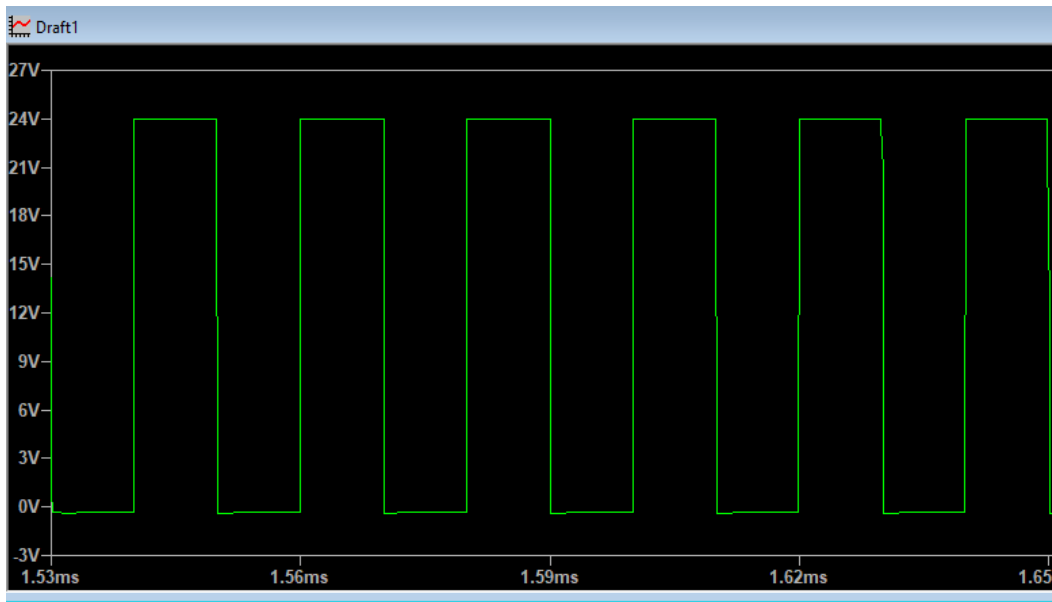


Fig 7: Voltage across the switching device and diode

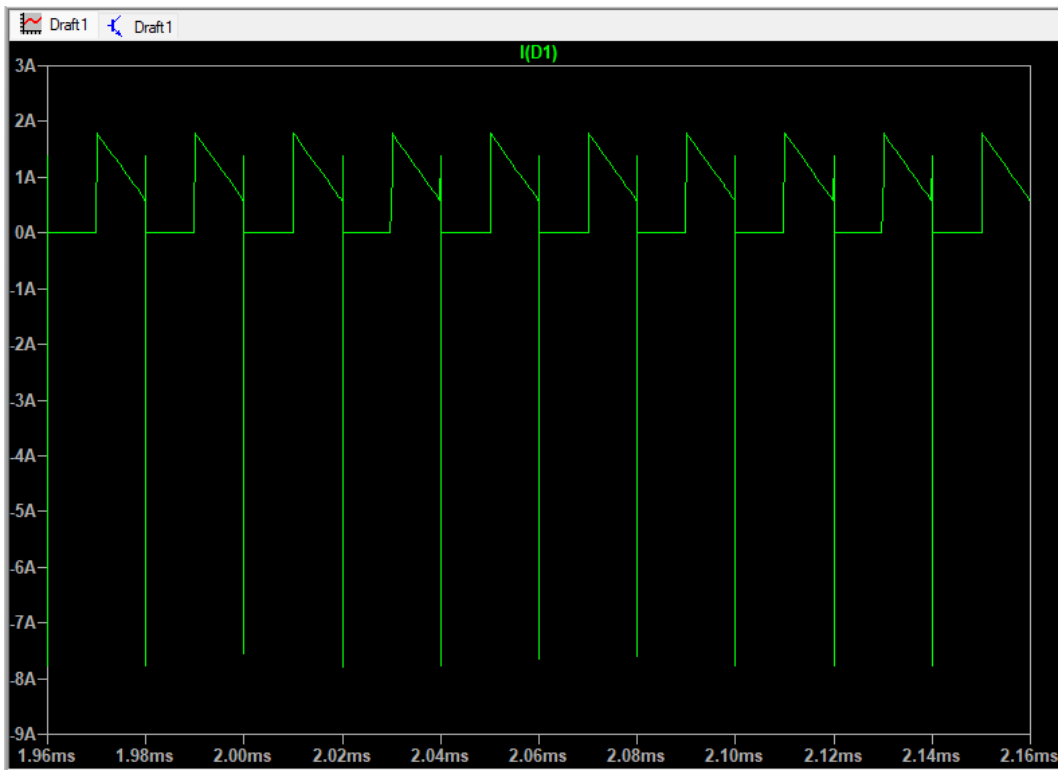


Fig 8: Current waveform across diode

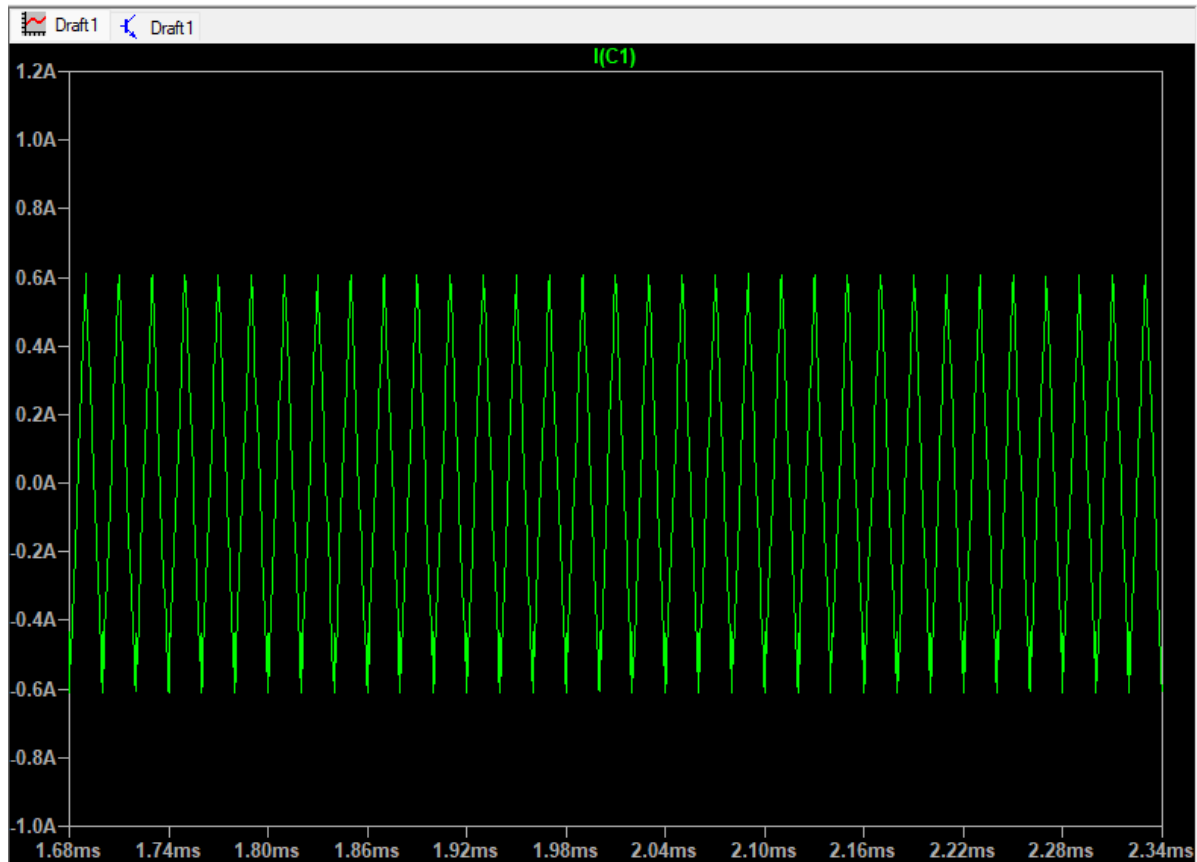


Fig 9: Current waveform across the capacitor

Efficiency of converter = $12/24 = 0.50 = 50\%$

PRACTICAL ANALYSIS (Done in Lab)

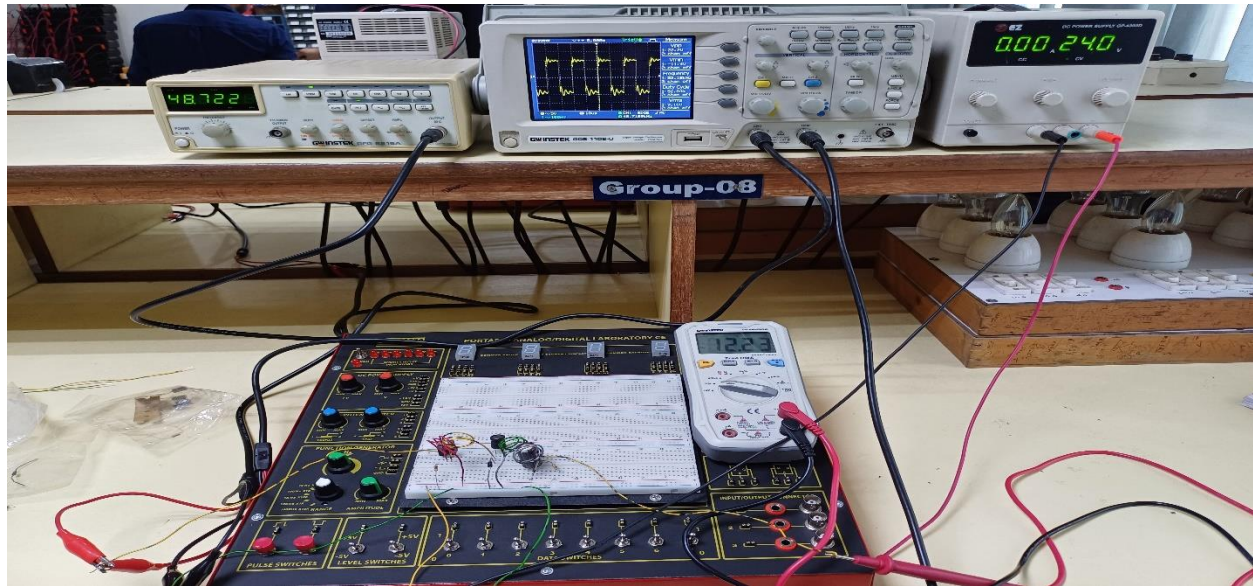


Fig 10: $V_{in} = 24.0 \text{ V}$ and $V_{out} = 12.23 \text{ V}$

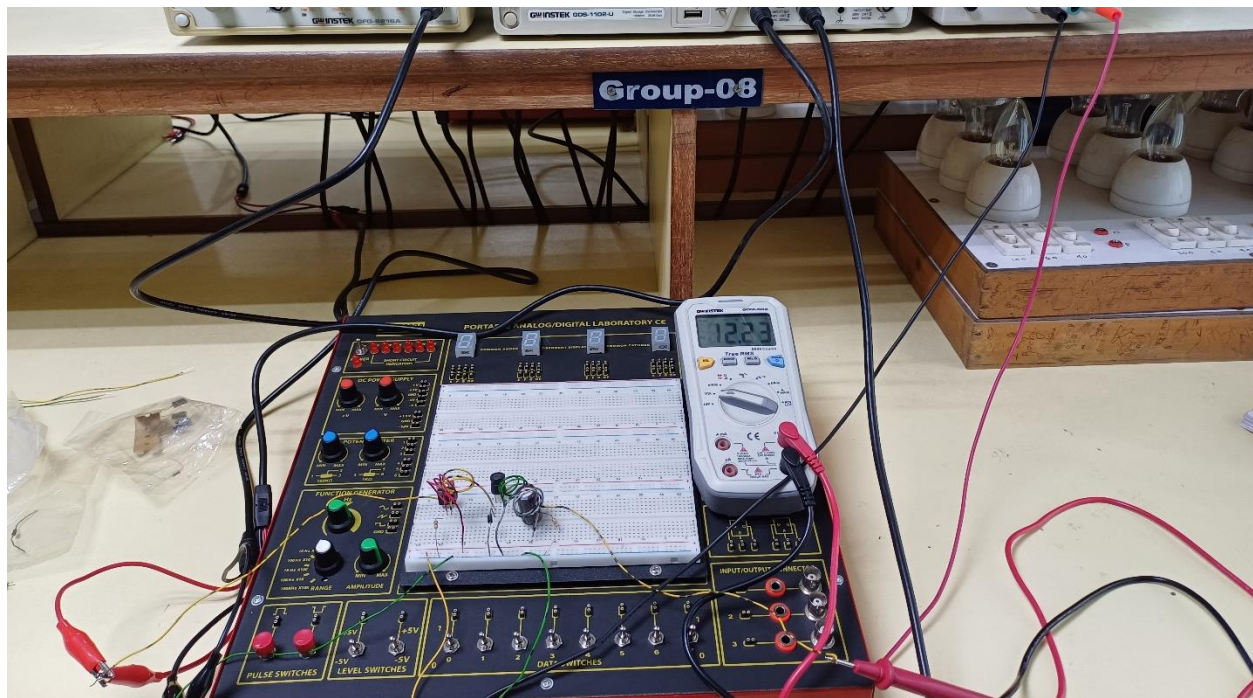


Fig 11: Buck Converter Circuit



Fig 12: Switching frequency and duty cycle

Here,

Input voltage, $V_{in} = 24.0V$

Output voltage, $V_{out} = 12.23 V$

Frequency of switching = 48.722 kHz

Duty cycle = 52.83% (From oscilloscope)

Efficiency = $1 - (12.23/24) = 0.49 = 49\%$

Comparison between Simulated values and practical results:

	Simulated values	Practical result	Error %
V_{in}	24 V	24 V	0
V_{out}	12 V	12.23 V	1.92
Switching frequency	50 kHz	48.722 Hz	2.56
Duty cycle	50%	52.83%	5.64
Efficiency	50%	49%	2%
Ripple voltage	0.23 V	0.2 V	13.04%
Ripple percentage	1.92%	1.64%	14.58%

Comment: Here we can see some difference between simulated and practical values. It happened because there is a difference in switching frequency. We could not find 10Ω 50W resistor. That is why we used $1k\Omega$ resistor and made necessary change in inductor value (30 μH)

Discussion:

In this project we made a buck converter. We can observe there are some differences in simulated values and practical values. The reasons are given below:

- 1) The equipment we used were not ideal case. Those equipment has some errors
- 2) The used frequency generator, oscilloscope and multimeter also have errors
- 3) We could not find any 10Ω 50W resistor in the market. So, we used $1k\Omega$ resistor and used a 30uH inductor instead of 100uH

Video link of the project

https://drive.google.com/file/d/1A6YVaiPHam7MV-TO0s1GLhCnoP3sUD95/view?usp=drive_link